

Computer Logic 1 – Practical 1


Objective:

To use the *Xilinx ISE Design Suite* to simulate simple combinational circuits.


Tasks:

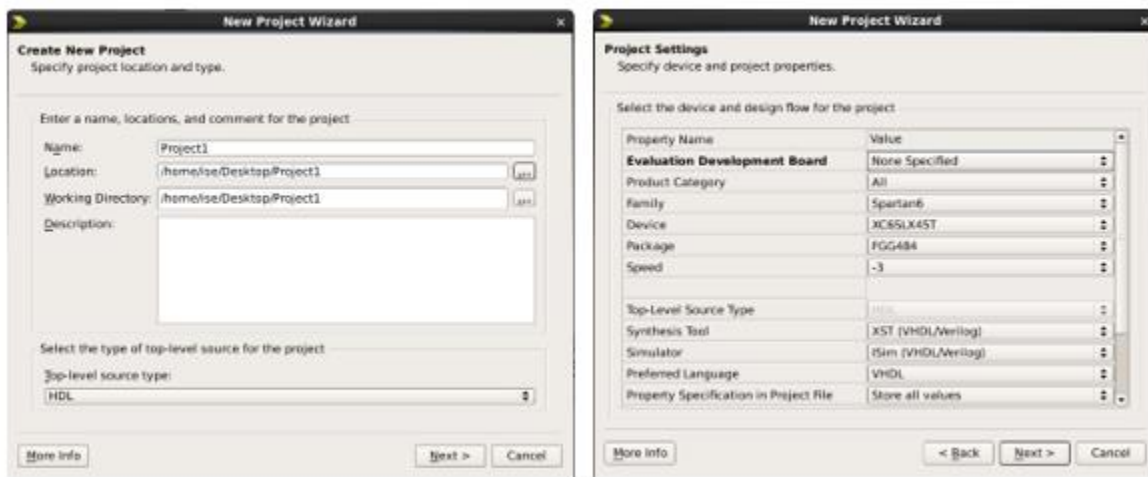- 1) The *Xilinx ISE environment* was opened on the Linux virtual machine and a new project was created using the menu item *File ~> New Project*. The project was then called “*Project1*” and it was set to be stored in a particular location. Then, the following options were chosen (whilst others were left unchanged):

- Top-level source type: HDL
- Family: Spartan6
- Device: XC6SLX45T
- Package: FGG484
- Synthesis tool: XST (VHDL/Verilog)
- Simulator: Isim (VHDL/Verilog)
- Preferred language: VHDL



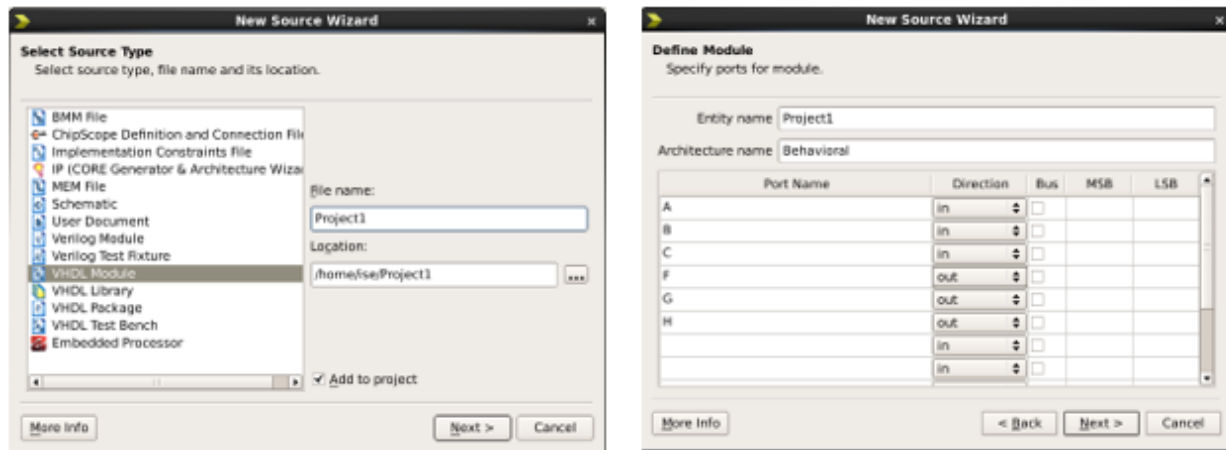- 2) A new source file was then created using the menu item *Project ~> New Source*. The new source was of type VHDL Module and 3 input(A, B, C) and another 3 output(F, G, H) ports were assigned as shown.



- 3) In the architecture body, VHDL code was added to set the inputs to correspond to Truth Table 1. The truth table and code inputted are shown below:

TABLE 1: TRUTH TABLE.


| <i>A</i> | <i>B</i> | <i>C</i> | <i>F</i> | <i>G</i> | <i>H</i> |
|----------|----------|----------|----------|----------|----------|
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 |

```

architecture Behavioral of VHDLmodule1 is
begin
  F <= (not A and not B and not C)
        or (not A and B and C)
        or (A and not B and C);
  G <= (not A and not B and C)
        or (not A and B and not C)
        or (A and not B and not C)
        or (A and B and C);
  H <= (not A and not B and not C)
        or (not A and not B and C)
        or (not A and B and C)
        or (A and not B and not C)
        or (A and not B and C);
end Behavioral;

```

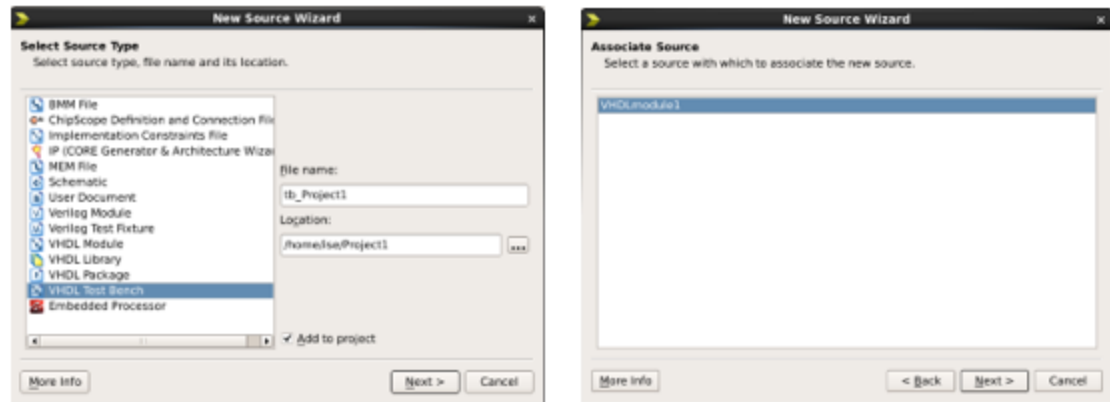- 4) After the VHDL code was entered, functional simulation was performed. This was done by generating a test bench:
- A new file called *tb_Project1* was created from menu item *Project ~> New Source*. The source type was set to *VHDL Test Bench* and the original VHDL file *Project1* was associated with this newly created one.



- b) Parts of the test bench usually used for clock were eliminated as they were irrelevant to this particular design.
- c) The stimulus process was replaced with the following code:

```
a_proc: process
begin
    A <= '0';
    wait for 200 ns;

    A <= '1';
    wait for 200 ns;
end process;
```

- d) Other processes were then written to stimulate B and C as shown:

| | |
|--|--|
| <pre>b_proc: process begin B <= '0'; wait for 100 ns; B <= '1'; wait for 100 ns; end process;</pre> | <pre>c_proc: process begin C <= '0'; wait for 50 ns; C <= '1'; wait for 50 ns; end process;</pre> |
|--|--|

- 5) The *Simulation* view in the top left panel was then selected, followed by the *Behavioral* simulation. The test bench was then selected and the *Simulate Behavioral Model* option in the process panel was chosen.
- 6) The outputs were checked to correspond to *Truth Table 1*.
- 7) The test bench file was then modified with some artificial glitches and saved.

```

B <= '0';   to:  B <= '0' after 3 ns;
B <= '1';   to:  B <= '1' after 3 ns;
C <= '0';   to:  C <= '0' after 5 ns;
C <= '1';   to:  C <= '1' after 5 ns;

```

- 8) The design was simulated once more.
- 9) In this case, some glitches known as hazards were introduced. There were 2 types:
- a) Static hazards: Those having the same levels before and after (initial value '1', followed by short '0' and final value is '1' again)



- b) Dynamic hazards: Those having different levels before and after (initial value '0', followed by a short '1' and another short '0' and final value is '1')



These hazards were caused by the artificial glitches introduced in step 7.

An example of a static hazard in this Project would be: Outputs *F* and *G* between 100 – 110 ns.

An example of a static hazard in this Project would be: Outputs *F* and *G* between 190 – 210 ns.

Appendix (Code):

VHDL Module (Project1):

```
1 -----
2 -- Company:      UOM
3 -- Engineer:     Tristan Oa Galea
4 --
5 -- Create Date:  22:28:58 11/08/2018
6 -- Design Name:  Project 1
7 -- Module Name:  VHDLmodule1 - Behavioral
8 -- Project Name: Project 1
9 -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity VHDLmodule1 is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           C : in  STD_LOGIC;
36           F : out STD_LOGIC;
37           G : out STD_LOGIC;
38           H : out STD_LOGIC);
39 end VHDLmodule1;
40
41 architecture Behavioral of VHDLmodule1 is
42
43 begin
44     F <= (not A and not B and not C)
45         or (not A and B and C)
46         or (A and not B and C);
```

```
47
48 G <= (not A and not B and C)
49       or (not A and B and not C)
50       or (A and not B and not C)
51       or (A and B and C);
52
53 H <= (not A and not B and not C)
54       or (not A and not B and C)
55       or (not A and B and C)
56       or (A and not B and not C)
57       or (A and not B and C);
58 end Behavioral;
```

VHDL Test Bench (tb_Project1):


```

1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    22:40:25 11/08/2018
6  -- Design Name:
7  -- Module Name:    /home/ise/Project1/tb_Project1.vhd
8  -- Project Name:   Project1
9  -- Target Device:
10 -- Tool versions:
11 -- Description:
12 --
13 -- VHDL Test Bench Created by ISE for module: VHDLmodule1
14 --
15 -- Dependencies:
16 --
17 -- Revision:
18 -- Revision 0.01 - File Created
19 -- Additional Comments:
20 --
21 -- Notes:
22 -- This testbench has been automatically generated using types std_logic and
23 -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
24 -- that these types always be used for the top-level I/O of a design in order
25 -- to guarantee that the testbench will bind correctly to the post-implementation
26 -- simulation model.
27  -----
28  LIBRARY ieee;
29  USE ieee.std_logic_1164.ALL;
30
31  -- Uncomment the following library declaration if using
32  -- arithmetic functions with Signed or Unsigned values
33  --USE ieee.numeric_std.ALL;
34
35  ENTITY tb_Project1 IS
36  END tb_Project1;
37
38  ARCHITECTURE behavior OF tb_Project1 IS
39
40      -- Component Declaration for the Unit Under Test (UUT)
41
42      COMPONENT VHDLmodule1
43      PORT (
44          A : IN  std_logic;
45          B : IN  std_logic;
46          C : IN  std_logic;
47          F : OUT std_logic;
48          G : OUT std_logic;
49          H : OUT std_logic;
50      );
51      END COMPONENT;
52
53      --Inputs
54      signal A : std_logic := '0';
55      signal B : std_logic := '0';
56      signal C : std_logic := '0';

```

```
57
58     --Outputs
59     signal F : std_logic;
60     signal G : std_logic;
61     signal H : std_logic;
62     -- No clocks detected in port list. Replace <clock> below with
63     -- appropriate port name
64
65 BEGIN
66
67     -- Instantiate the Unit Under Test (UUT)
68     uut: VHDLmodule1 PORT MAP (
69         A => A,
70         B => B,
71         C => C,
72         F => F,
73         G => G,
74         H => H
75     );
76
77     a_proc: process
78     begin
79         A <= '0';
80         wait for 200 ns;
81
82         A <= '1';
83         wait for 200 ns;
84     end process;
85
86     b_proc: process
87     begin
88         B <= '0' after 3 ns;
89         wait for 100 ns;
90
91         B <= '1' after 3 ns;
92         wait for 100 ns;
93     end process;
94
95     c_proc: process
96     begin
97         C <= '0' after 5 ns;
98         wait for 50 ns;
99
100        C <= '1' after 5 ns;
101        wait for 50 ns;
102    end process;
103
104 END;
```

 
Simulated Behavioral Model: (With glitches)



Conclusion:

Xilinx ISE Design Suite was successfully used to simulate simple combinational circuits.